

02207 : Advanced Digital Design Techniques

Lab 1: Exercise on Synthesis

Group *dt07*

Markku Eerola (s053739)

Rajesh Bachani (s061332)

Josep Renard (s071158)

October 23, 2007

Contents

1	Purpose of the Exercise	2
2	Behavioral Description for 24-bit Adder	2
2.1	VHDL code for the 24-bit Adder	2
2.2	Simulation with Modelsim	2
3	Behavioral Description for 24-bit Register	4
4	Top-Level Netlist from 24-bit Adder and 24-bit Register	4
5	Synthesis Results	5
5.1	Clock Time Period = 0.5 ns	6
5.2	Clock Time Period = 1.0 ns	7
5.3	Clock Time Period = 2.0 ns	8
5.4	Comments	9

1 Purpose of the Exercise

The goal of the exercise was to get familiar with the process of synthesis of digital circuits, using special tools for synthesis such as Design Vision. A register-level netlist containing a 24-bit adder is synthesized in the exercise, for different values of the clock time period. The reports concerning the timing constraints, area, power consumption etc. which are generated by the tool are documented in the report.

2 Behavioral Description for 24-bit Adder

2.1 VHDL code for the 24-bit Adder

The VHDL code for a simple 24-bit adder is provided below.

```
library IEEE;
use IEEE.std_logic_1164.all, IEEE.numeric_std.all;

entity NBitAdder is
    port (A, B: in std_logic_vector(23 downto 0);
          Cin: in std_logic;
          Sum: out std_logic_vector(23 downto 0);
          Cout: out std_logic);
end entity NBitAdder;

architecture unsngned of NBitAdder is
    signal result: unsigned(24 downto 0);
    signal carry: unsigned(24 downto 0);
    constant zeros: unsigned(23 downto 0) := (others => '0');

begin
    carry <= (zeros & Cin);
    result <= ('0' & unsigned(A)) + ('0' & unsigned(B)) + carry;
    Sum <= std_logic_vector(result(23 downto 0));
    Cout <= result(24);
end architecture unsngned;
```

2.2 Simulation with Modelsim

The behavior of this adder is verified in Modelsim. Following is a testbench for the adder, and also a screenshot for the waveform from the values provided by the testbench.

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity TestNBitAdder is
end entity TestNBitAdder;


architecture TestBench_4 of TestNBitAdder is
    signal A, B, Sumint : NATURAL;
    signal Aslv, Bslv, Sum: std_logic_vector (23 downto 0);
    signal Cin, Cout: std_logic;
    signal error: BOOLEAN := FALSE;
```

```

begin
s0: entity WORK.NBitAdder(unsigned) port map(Aslv , Bslv , Cin , Sum, Cout);
Aslv <= std_logic_vector(to_unsigned(A, 24));
Bslv <= std_logic_vector(to_unsigned(B, 24));
Sumint <= to_integer(unsigned(Cout & Sum));
stim: process is
begin
Cin <= '0';
A <= 44;
B <= 8990;
wait for 5 NS;
A <= 34545;
wait for 5 NS;
Cin <= '1';
wait for 5 NS;
A <= 7840;
wait for 5 NS;
B <= 0;
wait for 5 NS;
Cin <= '0';
wait;
end process;

resp: process (Cout, Sum) is
begin
error <= (A + B + BIT'POS(to_bit(Cin))) /= Sumint;
end process;
end architecture TestBench_4;

```

 

As we can see, the values of a, b and cin at the point of the yellow line are 34545, 8990 and 1. The resulting sum is shown as 43536, which is correct. Even for the other values in the testbench, we can verify the adder is working fine.

3 Behavioral Description for 24-bit Register

The VHDL code for a 24-bit register is provided below.

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity reg is
port (D : in std_logic_vector(23 downto 0);
Clock, Reset : in std_logic;
Q : out std_logic_vector(23 downto 0));
end entity reg;

architecture behavioural of reg is
begin
p0: process (Clock, Reset) is
begin
if (Reset = '0') then
Q <= (others => '0');
elsif rising_edge(Clock) then
Q <= D;
end if;
end process p0;
end architecture behavioural;
```

4 Top-Level Netlist from 24-bit Adder and 24-bit Register

The VHDL code for the top-level netlist described in the exercise sheet, is provided below.

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity AdderNetlist is
port( A1 : in std_logic_vector(23 downto 0);
A2 : in std_logic_vector(23 downto 0);
Clock, Reset: in std_logic;
Z : out std_logic_vector( 23 downto 0));
end entity AdderNetlist;

architecture NetlistBehavior of AdderNetlist is
component NBitAdder is
port (A, B: in std_logic_vector(23 downto 0);
Cin: in std_logic;
Sum: out std_logic_vector(23 downto 0);
Cout: out std_logic);
end component NBitAdder;

component reg is
port (D : in std_logic_vector(23 downto 0);
Clock, Reset : in std_logic;
Q : out std_logic_vector(23 downto 0));
```

```

end component reg;

    signal Co, Ci : std_logic;
    signal A1out, A2out, Sum : std_logic_vector(23 downto 0);
    begin
        g1: reg port map (A1, Clock, Reset, A1out);
        g2: reg port map (A2, Clock, Reset, A2out);
        g3: nbitadder port map (A1out, A2out, Ci, Sum, Co);
        g4: reg port map (Sum, Clock, Reset, Z);
    end architecture NetlistBehavior;

```

5 Synthesis Results

The synthesis of the top-level netlist described in section 4 is done using Design Vision by Synopsys. We have synthesized the netlist for three different sets of clock time periods, which are 0.5, 1.0 and 2.0 ns. For each of these time periods, we have synthesized the netlist with and without constraints for low power. In the end, we have commented on the results obtained from the data gathered.

The power constraints for low power are 1 uW and 1 pW for maximum dynamic power and maximum leakage power respectively. This is done by using the following two commands (as is also shown in the exercise sheet):

```

set_max_dynamic_power 1
set_max_leakage_power 1

```

For the synthesis in which no constraints are put on power, the values are kept at 10 mW and 30 uW for maximum dynamic power and maximum leakage power respectively.

```

set_max_dynamic_power 10 mW
set_max_leakage_power 30 uW

```

In the following subsections, we give the results and comments of the synthesis for both the above mentioned power constraints. In the next section, we give comments for the change in area and power with respect to the different clock periods.

5.1 Clock Time Period = 0.5 ns

Parameters	Values	Comment
Dynamic Power	5.91 mW	MET
Leakage Power	11.04 uW	MET
Library Setup Time	0.08 ns	-
Data Arrival Time	0.43 ns	-
SLACK	-0.01 ns	VIOLATED
Combinational Area	2700 μm^2	-
Non-Combinational Area	1343 μm^2	-
SVT cells	403	-
HVT cells	0	-

Table 1:

Synthesis for low power:

Parameters	Values	Comment
Dynamic Power	5.29 mW	VIOLATED
Leakage Power	9.22 uW	VIOLATED
Library Setup Time	0.08 ns	-
Data Arrival Time	0.44 ns	-
SLACK	-0.02 ns	VIOLATED
Combinational Area	2345 μm^2	-
Non-Combinational Area	1343 μm^2	-
SVT cells	377	-
HVT cells	0	-

Table 2:

5.2 Clock Time Period = 1.0 ns

Parameters	Values	Comment
Dynamic Power	2.76 mW	MET
Leakage Power	11.25 uW	MET
Library Setup Time	0.08 ns	-
Data Arrival Time	0.89 ns	-
SLACK	0.02 ns	MET
Combinational Area	2335 um ²	-
Non-Combinational Area	1343 um ²	-
SVT cells	276	-
HVT cells	0	-

Table 3:

Synthesis for low power:

Parameters	Values	Comment
Dynamic Power	1.71 mW	VIOLATED
Leakage Power	2.98 uW	VIOLATED
Library Setup Time	0.09 ns	-
Data Arrival Time	0.90 ns	-
SLACK	0.00 ns	MET
Combinational Area	1089 um ²	-
Non-Combinational Area	1343 um ²	-
SVT cells	205	-
HVT cells	0	-

Table 4:

5.3 Clock Time Period = 2.0 ns

Parameters	Values	Comment
Dynamic Power	0.896 mW	MET
Leakage Power	3.51 uW	MET
Library Setup Time	0.09 ns	-
Data Arrival Time	1.87 ns	-
SLACK	0.05 ns	MET
Combinational Area	631 μm^2	-
Non-Combinational Area	1343 μm^2	-
SVT cells	97	-
HVT cells	0	-

Table 5:

Synthesis for low power:

Parameters	Values	Comment
Dynamic Power	0.88 mW	MET
Leakage Power	3.17 uW	VIOLATED
Library Setup Time	0.09 ns	-
Data Arrival Time	1.91 ns	-
SLACK	0.00 ns	MET
Combinational Area	614 μm^2	-
Non-Combinational Area	1343 μm^2	-
SVT cells	97	-
HVT cells	0	-

Table 6:

5.4 Comments

Comments for synthesis results for low-power:

- For low power, the tool has tried to reduce the power to some extent. In some cases the constraint for the maximum dynamic power is met, while the constraint for maximum leakage power is never met.
- The little reduction in the power with the low power constraints, is achieved by reducing the number of SVT cells in the design. This is because the SVT cells take more power as compared to the HVT cells. But since these cells are faster, reducing their number increases the delay in the circuit, as can be seen by an increase in the time of data arrival for all the three cases.
- The combinational area reduces when synthesizing for low power. (Why?)
- We would have expected to see an increase in the number of HVT cells when synthesis is performed for low power, but it has not been the case. This is expected since the HVT cells take less power and also the number of SVT cells has decreased for low power.

Comments on variations observed by changing the clock time-period:

- The design is not synthesized successfully for the clock time period of 0.5 ns. The critical path in this case for the adder is 0.43 ns and adding the register setup and propagation delay time, the total time delay becomes greater than 0.5 ns. However, we see that the circuit is successfully synthesized for timing constraints of 1.0 ns and 2.0 ns.
- The number of cells decreases with the increasing clock time period. So, as the constraint on the time period is reduced, the circuit is synthesized with lower number of cells. This is because the design is moving from parallel to sequential with an increase in clock time period constraint.
- The area for the non-combinational circuit remains the same in all the cases. This is expected since the non-combinational circuit consists of three registers, which would have the same internal design on synthesis. The synthesis is mainly done for the internal design of the 24-bit adder, depending on the constraints of clock time period.
- The area for the combinational circuit decreases with the increasing clock time period. This is because the number of cells decreases in the synthesized circuit.
- The total power, including the dynamic power and the leakage power, decreases as the clock time period is increased. Again, the reason for this is the decrease in the number of cells.